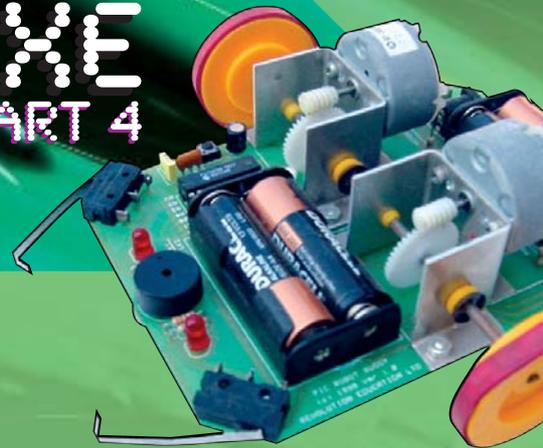


PRACTICAL PICAXE

PART 4



Controlling Motors

John Cook builds on his previous article on motor control and takes us a step further with some useful ways to control and drive motors in robot vehicles using PICAXE and some practical advice on motors. All the circuits can also be found for this and previous articles on the TEP website at www.tep.org.uk





My first introduction to PIC's was a one-day course, run by Clive Seagar, where we built and programmed a buggy using the then new Chip Factory. I was struck by the ease with which programmes could be produced and downloaded. Shortly after, I ran a few INSET sessions for TEP using some loaned Chip Factories and buggies. Whilst I had the kit I decided to see what impact PIC's would have with my year 10 System and Control Pupils just before they were about to begin their major projects. This very quick introduction resulted in the pupils deciding to go 100% down the PIC route, establishing the norm for years to follow. There is still a lot of mileage to be gained from buggies and walkers. My recent experience with year 9 pupils at Harper Adams, article in last News & Views, reminded me of the fun and excitement that these projects can develop.

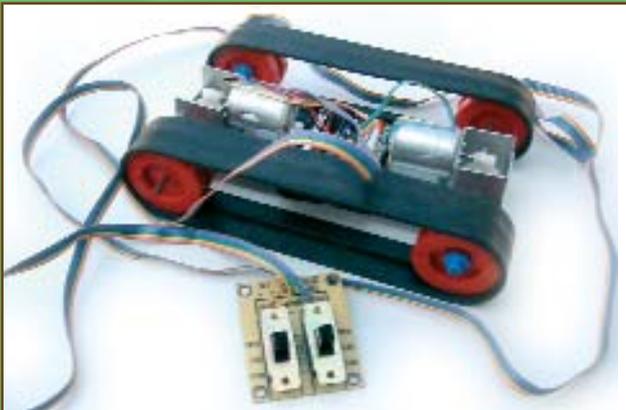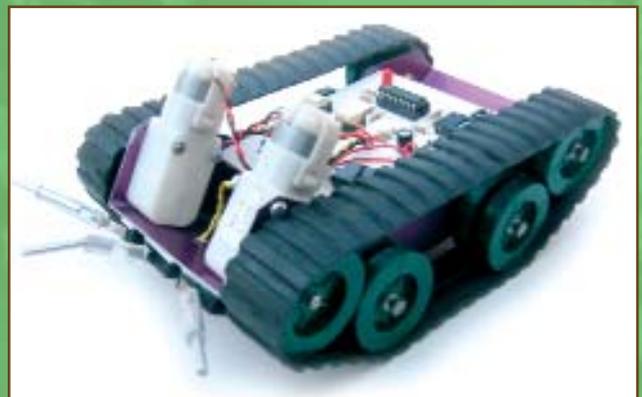The next logical step was to produce a vehicle that can operate independently, removing the need for the umbilical. This would demonstrate clear progression and offer the potential for extension work.



My last article introduced motor control via a motor driver chip, L293D and used an opto-isolator to prevent noise from stopping the PIC Programme running correctly. In order to access top marks at GCSE controlling one motor is sufficient, using one half of the L293D, but in order to steer a vehicle requires two motors thus utilising the motor driver to its full. The PCB Wizard example shows the full use of the L293D chip and two opto-isolator chips. Whilst it is possible to buy a quad opto-isolator, I prefer to limit the number of different components used.

TEP produce this Magic of Engineering tracked vehicle operated via an umbilical wire from two double pole double throw switches. The original design was great in straight lines but tight turns were impossible due to the amount of friction produced by the tracks. After a bit of product analysis, pupils quickly decided upon various solutions, such as the one below which will turn on the spot, is fairly fast and fun to drive over various terrains.

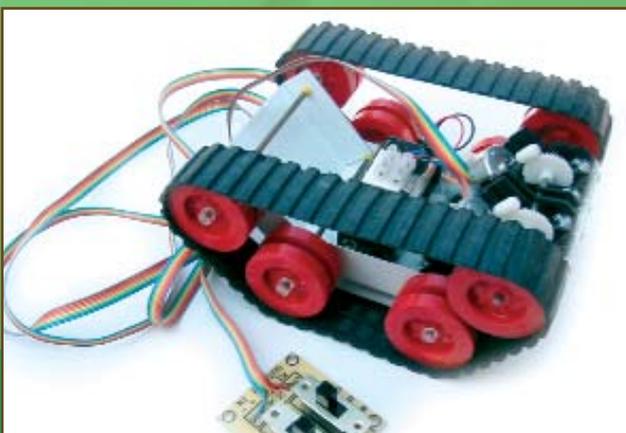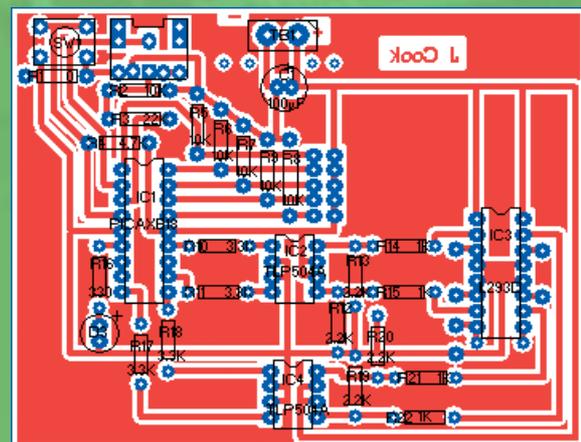

There are a couple of small points worth mentioning, pin 8 and 9 of the motor driver chip are coupled together with a wire link to provide the same battery supply to each motor using the pads below the pins. The pad joined to the left of pin 8 allows for a separate power supply positive connection and the pad directly below the 0v connection.

